

CS M51A, Fall 2022, Assignment 3
 (Total Mark: 100 points, 10%)

Due: Fri Nov 11, 10:00 AM Pacific Time

Student Name: *Yash Shah*


Student ID: *405-565-567*

Note: You must complete the assignments entirely on your own,
 without discussing with others.

- Given the following table:

A	B	C	F
x_2	x_1	x_0	
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

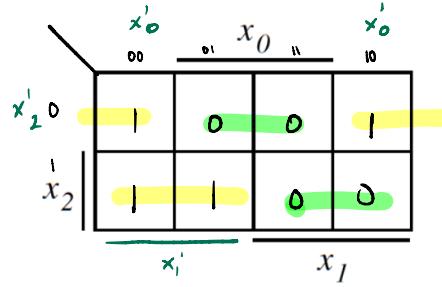- (4 points) Fill out the k-maps for this table.



- (4 points) Write the minimal **sum of products** for F.

$$F_{\text{SOP}} = x_1' x_2 + x_0' x_2'$$


- (4 points) Write the minimal **product of sums** for F.

$$F_{\text{POS}} = (x_2' + x_0')(x_1 + x_2')$$

$$F_{\text{POS}} = (x_2 + x_0)(x_1' + x_2')$$

2. Given $f(x_3, x_2, x_1, x_0) = x_3x_2x_1x'_0 + x_3x_2x_1x_0 + x'_3x_2x_1x_0 + x'_3x_2x_1x_0 + x'_3x_2x_1x'_0 +$

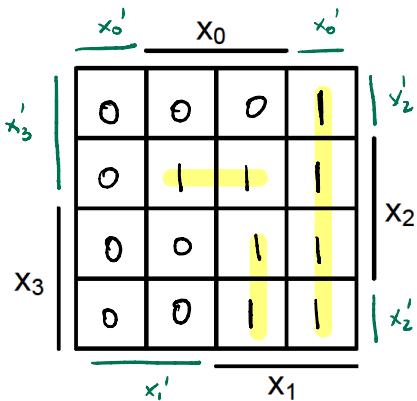
(a) (8 points) Fill out the following K-maps.



(b) (4 points) Write the minimal sum of products expression for f .


$$F = x_0x_3'x_2 + x_3x_1 + x_0'x_1$$

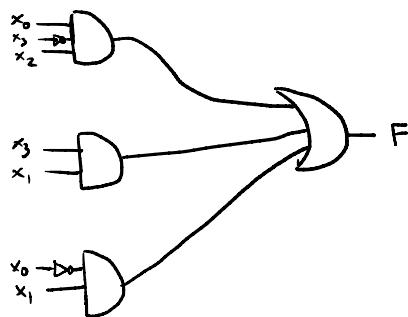(c) (4 points) Draw the gate level design for (b)



3. Using K-maps, find the minimal SOP and POS that are equivalent to the following expressions ($dc(\dots)$ indicates the "don't care" terms):

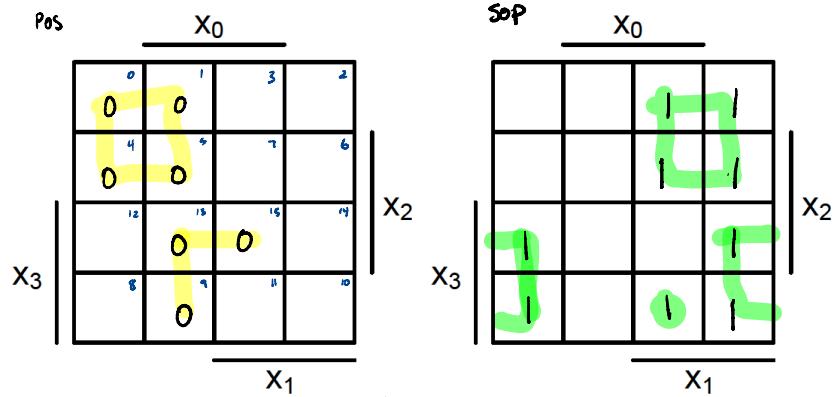(a) (10 Points) $F(x_3, x_2, x_1, x_0) = \Pi M(0, 1, 4, 5, 9, 13, 15)$




$$F_{POS} = (x_3' + x_1') + (x_1' + x_0') + (x_1 + x_3 + x_2)$$

$$F_{POS} = (x_3' + x_1)(x_1 + x_0')(x_0' + x_2' + x_3')$$

$$F_{SOP} = (x_1 x_3') + (x_3 x_0') + (x_1 x_2)$$

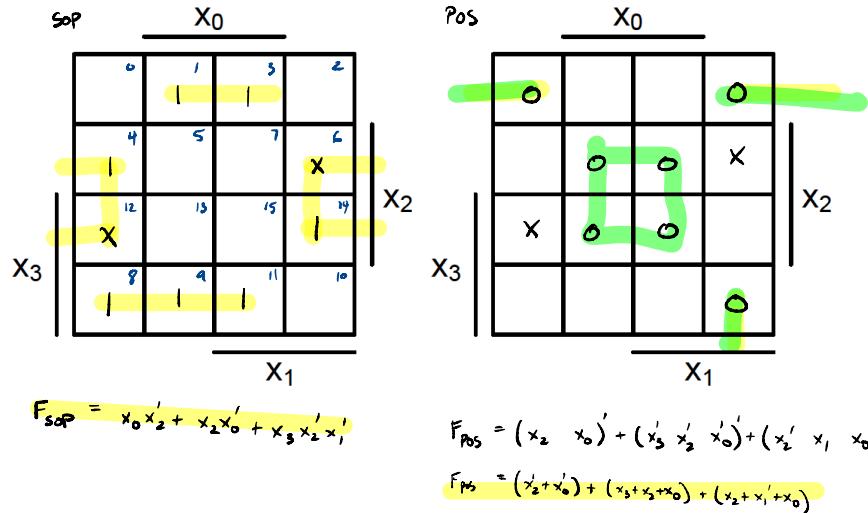(b) (10 Points) $F(x_3, x_2, x_1, x_0) = \Sigma m(1, 3, 4, 8, 9, 11, 14), dc(x_3, x_2, x_1, x_0) = \{m(6), m(12)\}$



$$F_{SOP} = x_0 x_2' + x_2 x_0' + x_3 x_2 x_1'$$

$$F_{POS} = (x_2 - x_0)' + (x_3' x_2' x_0') + (x_2' - x_1 - x_0)'$$

$$F_{POS} = (x_2' + x_0') + (x_3 + x_2 + x_0) + (x_2 + x_1' + x_0)$$

4. (6 Points) Determine whether the sequential systems described by the following tables corresponds to Moore or Mealy machines.

	Input	
PS	$x = 0$	$x = 1$
A	$C, 1$	$B, 1$
B	$\textcircled{A, 1}$	$\textcircled{C, 0}$
C	$A, 1$	$B, 1$
	NS, Output	

$\text{Input} \neq \text{Output}$

Mealy

	Input	
PS	$x = 0$	$x = 1$
A	$B, 0$	$A, 0$
B	$B, 1$	$C, 1$
C	$A, 1$	$B, 1$
	NS, Output	

$\text{Input} = \text{output}$

Moore

	Input	
PS	$x = 0$	$x = 1$
A	$A, 0$	$B, 0$
B	$A, 1$	$C, 1$
C	$A, 1$	$D, 0$
D	$A, 0$	$A, 0$
	NS, Output	

$\text{Input} \neq \text{output}$

Mealy

$\text{Input} \neq \text{Output} \Rightarrow \text{output depends on state and input} \Rightarrow \text{mealy}$

$\text{Input} = \text{output} \Rightarrow \text{output depends on only state} \Rightarrow \text{moore}$

5. Consider the following state table:

PS	Input				NS, z
	x = a	x = b	x = c	x = d	
A	G, 1	E, 0	G, 1	C, 0	— A
B	D, 0	G, 0	E, 0	F, 1	— B
C	E, 1	G, 0	F, 1	A, 0	— C
D	E, 1	G, 0	F, 1	C, 0	— D
E	C, 0	G, 0	E, 0	F, 1	— E
F	C, 1	B, 1	A, 0	B, 1	— F
G	C, 0	E, 0	G, 0	F, 1	— G
H	G, 1	E, 0	F, 1	A, 0	— H

(a) (8 Points) Answer True or False for the questions:

- State C and D are 2-equivalent. **T**
- State A and H are 1-distinguishable. **F**
- State B and F are 1-equivalent. **F**
- State E and G are 1-distinguishable. **F**

(b) (8 Points) Simplify this table by reducing the state set as much as possible

P ₁	1 A C D H	2 B E G	3 F
a	2 2 2 2	1 1 1	
b	2 2 2 2	2 2 2	
c	2 3 3 3	2 2 2	
d	1 1 1 1	3 3 3	
u	[]		


P ₂	1 A	2 C D H	3 B E G	4 F
a	3 3 3	2 2 2		
b	3 3 3	3 3 3		
c	4 3 4	3 3 3		
d	1 4 1	4 4 4		

P ₃	1 A	2 D	3 C H	4 B E G	5 F
a			4 4	2 3 3	
b			4 4	4 4 4	
c			5 5	4 4 4	
d			1 1	5 5 5	

P ₄	1 A	2 D	3 C H	4 E G	5 B	6 F
			4 4	3 3		
			4 4	4 4		
			6 6	4 4		
			1 1	6 6		


(A) (D) (C, H) (E, G) (B) (F)

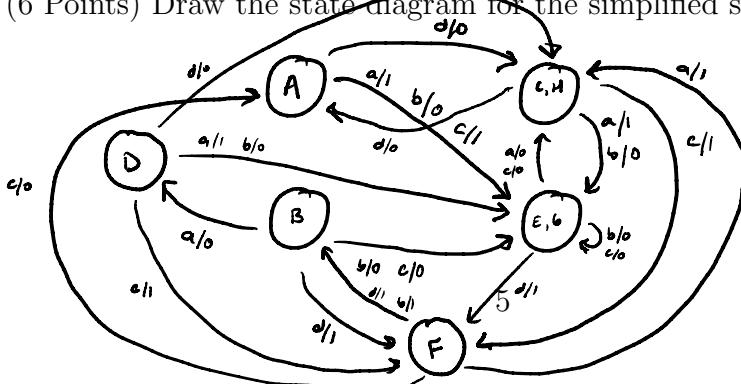(c) (6 Points) Draw the state diagram for the simplified state table.




6. (6 Points) Consider a sequential system that has a input $x(t) \in \{0, 1, 2, 3, 4, 5, 6, 7, 8, 9\}$ and one bit as output $y(t) \in \{0, 1\}$. The output is one if the number of times the pattern 53 has occurred in $x(0, t)$ is even. Otherwise, the output is zero. Show the state diagram of the system.

if ε represents the end of input

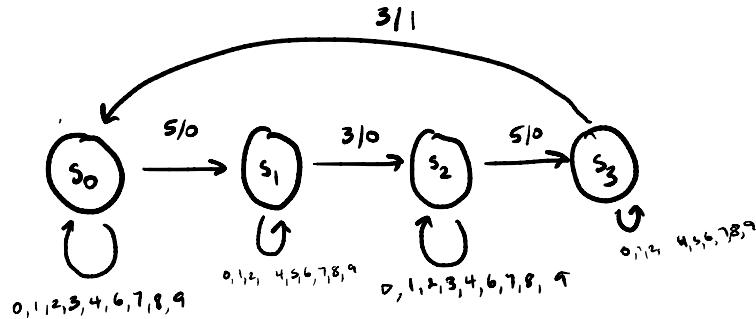

7. (10 Points) Consider the following next-state table and corresponding output table below. The inputs are C and D; the outputs are R and M. NS presents the next state, and $S = (S_1, S_0)$ presents current state. Draw the state diagram of the system using binary coding specification. Note that the X's are don't cares.

S_1	S_0	C	D	NS_1	NS_0	R	M
00	0	0	0	X	0	0	0 1
	0	0	1	0	1	0	0 1
	0	0	1	1	0	1	0 1
01	0	1	0	0	1	1	1 1
	0	1	0	1	1	1	1 1
	0	1	X	0	1	1	0 0
	0	1	1	1	0	0	1 1
10	1	0	0	X	1	0	0 0
	1	0	1	X	1	1	0 0
11	1	1	X	X	0	0	1 1

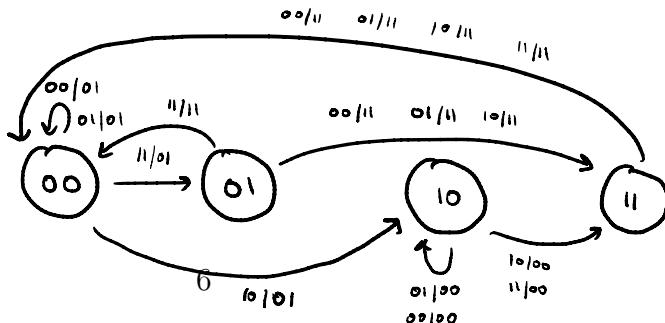

8. Simplify the following state tables by reducing the state set as much as possible.

(a) (4 Points)

PS	Input	
	$x = 0$	$x = 1$
a	$f, 0$	$b, 0$
b	$d, 0$	$c, 0$
c	$f, 0$	$e, 0$
d	$g, 1$	$a, 0$
e	$d, 0$	$c, 0$
f	$f, 1$	$b, 1$
g	$g, 0$	$h, 1$
h	$g, 1$	$a, 0$

P_1	Input				
	1	2	3	4	5
0	$a b c e$	$o h$	f	g	
1	$z z z z$	$4 4$			

P_2	Input				
	1	2	3	4	5
0	$a c$	$b e$	$o h$	f	g
1	$4 4$	$3 3$	$5 5$		

$$P = (a, c) (b, e) (o, h) (f) (g)$$

(b) (4 Points)

PS	Input			
	$x = a$	$x = b$	$x = c$	$x = d$
A	$E, 1$	$C, 0$	$B, 1$	$E, 1$
B	$C, 0$	$F, 1$	$E, 1$	$B, 0$
C	$B, 1$	$A, 0$	$D, 1$	$F, 1$
D	$G, 0$	$F, 1$	$E, 1$	$B, 0$
E	$C, 0$	$F, 1$	$D, 1$	$E, 0$
F	$C, 1$	$F, 1$	$D, 0$	$H, 0$
G	$D, 1$	$A, 0$	$B, 1$	$F, 1$
H	$B, 1$	$C, 0$	$E, 1$	$F, 1$

P_1	Input		
	1	2	3
a	$A G H C$	$B D E$	F
b	$2 2 2 2$	$1 1 1 1$	
c	$1 1 1 1$	$5 5 5 5$	
d	$2 2 2 2$	$2 2 2 2$	

P_2	Input			
	1	2	3	4
a	$3 3 3$	$2 2 2$		
b	$1 2 1$	$4 4 4$		
c	$3 3 3$	$5 5 5$		
d	$4 4 4$	$3 3 3$		

P_3	Input				
	1	2	3	4	5
a				$4 4$	$3 3 3$
b				$1 1$	$5 5 5$
c				$4 4$	$4 4 4$
d				$5 5$	$4 4 4$

$$P = (A) + (H) + (G, C) + (B, D, E) + F$$